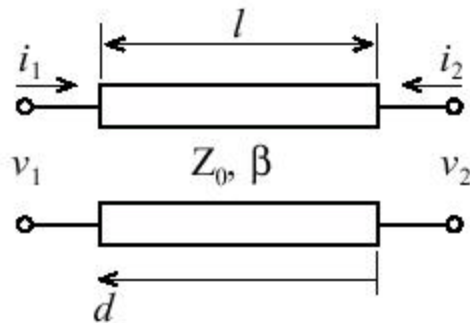


Stepped Impedance Low-Pass Filter

- Relatively easy (believe that?) low-pass implementation
- Uses alternating very high and very low characteristic impedance lines
- Commonly called Hi-Z, Low-Z Filters
- Electrical performance inferior to other implementations so often used for filtering unwanted out-of-band signals

Approximate Equivalent Circuits for Short Transmission line Sections

- Using Table 4-1, approximate equivalent circuits for a short length of transmission line with Hi-Z or Low-Z are found



$$A = \cos \beta l$$


$$C = \frac{j \sin \beta l}{Z_0}$$

$$B = jZ_0 \sin \beta l$$


$$D = \cos \beta l$$

Approximate Equivalent Circuits for Short Transmission line Sections


- The equivalent circuits are:

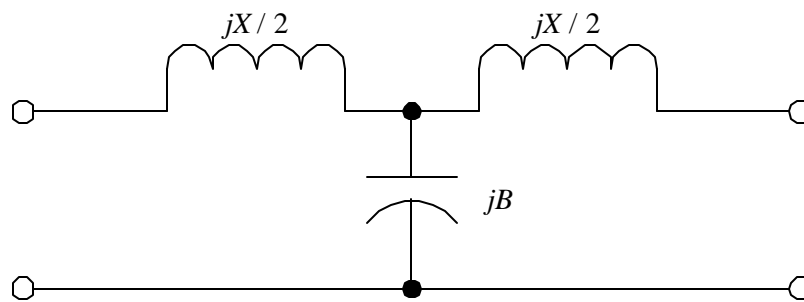

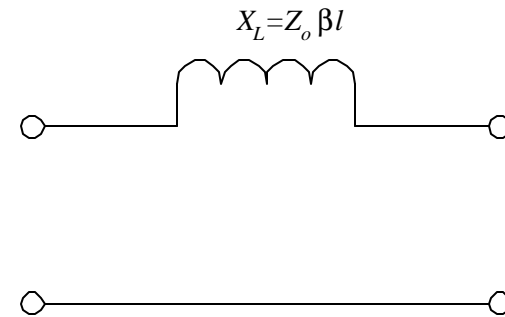T-Equivalent circuit for transmission line section
 $bl \ll \pi/2$



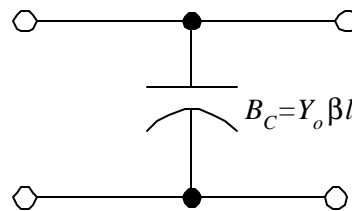Equivalent circuit for small bl and large Z_o



Equivalent circuit for small bl and small Z_o

Approximate Equivalent Circuits for Short Transmission line Sections

- Series inductors of a low-pass prototype replaced with Hi-Z line sections ($Z_o = Z_h$)
- Shunt capacitors replaced with Low-Z line sections ($Z_o = Z_l$)
- Ratio Z_h/Z_l should be as high as possible

$$bl = \frac{LR_g}{Z_h} \quad (\text{inductor})$$


$$bl = \frac{CZ_l}{R_g} \quad (\text{capacitor})$$

Stepped Impedance Low-Pass Filter


- Select the highest and lowest practical line impedance; e.g. the highest and lowest line impedances could be 150 and 10 Ω , respectively
- For example, given the low-pass filter prototype, solve for the lengths of the microstriplines:

$$l_{Ln} = g_n \frac{Z_{low}}{R_g \mathbf{b}} \quad ; \quad l_{Cn} = g_n \frac{R_g}{\mathbf{b} Z_{high}}$$

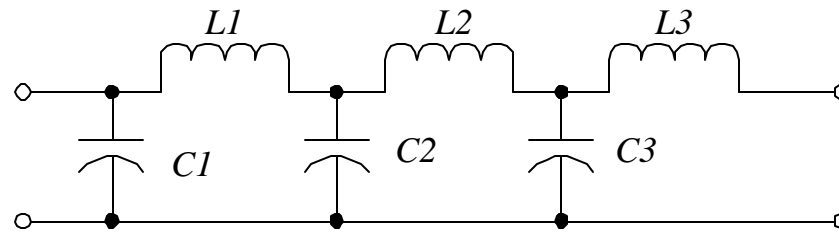Stepped Impedance Low-Pass Filter - Implementation



6th Order Low-Pass Filter Prototype

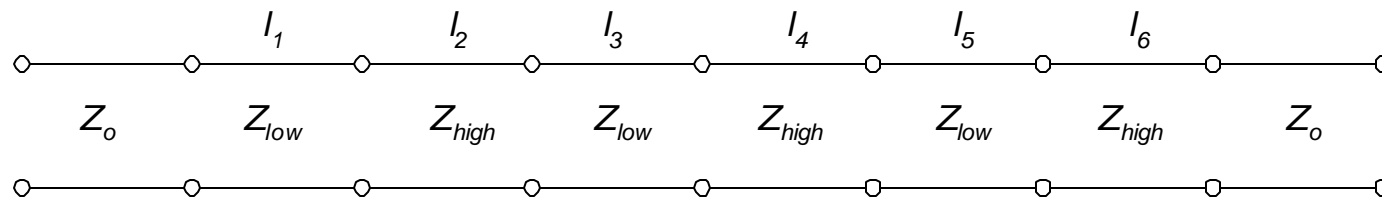

Stepped Impedance Implementation



Microstripline Layout of Filter

Bandstop Filter

- Require either maximum or minimal impedance at center frequency f_o
- Let line lengths $l = \lambda_o/4$
- Let $\Omega = 1$ cut-off frequency of the low-pass prototype transformed into upper and lower cut-off frequencies of bandstop filter via **bandwidth factor** :

$$bf = \cot\left(\frac{p}{2} \frac{w_L}{w_o}\right) = \cot\left[\frac{p}{2}\left(1 - \frac{sbw}{2}\right)\right] ; \quad sbw = \frac{(w_U - w_L)}{w_o}$$

Bandstop Filter: Implementation

1. Find the low-pass filter prototype
2. The L 's and C 's replaced by open and short circuit stubs, respectively as in Low-Pass filter design with


$$Z_{L_n} = (bf) g_n \text{ and } Y_{C_n} = (bf) g_n$$

3. Unit lengths of $\mathbf{l}_o/4$ are inserted and Kuroda's Identities are used to convert all series stubs into shunt stubs
4. Denormalize the unit elements


Coupled Filters: Bandpass

- Even and Odd mode excitations resulting in

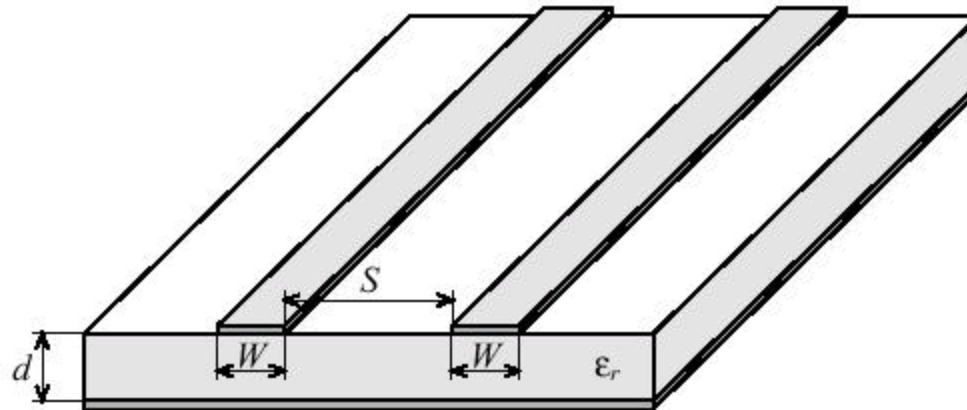
$$Z_{oe} = \frac{1}{v_{pe} C_e} \quad ; \quad Z_{oo} = \frac{1}{v_{po} C_{od}}$$



Coupled Filters: Even & Odd Impedances

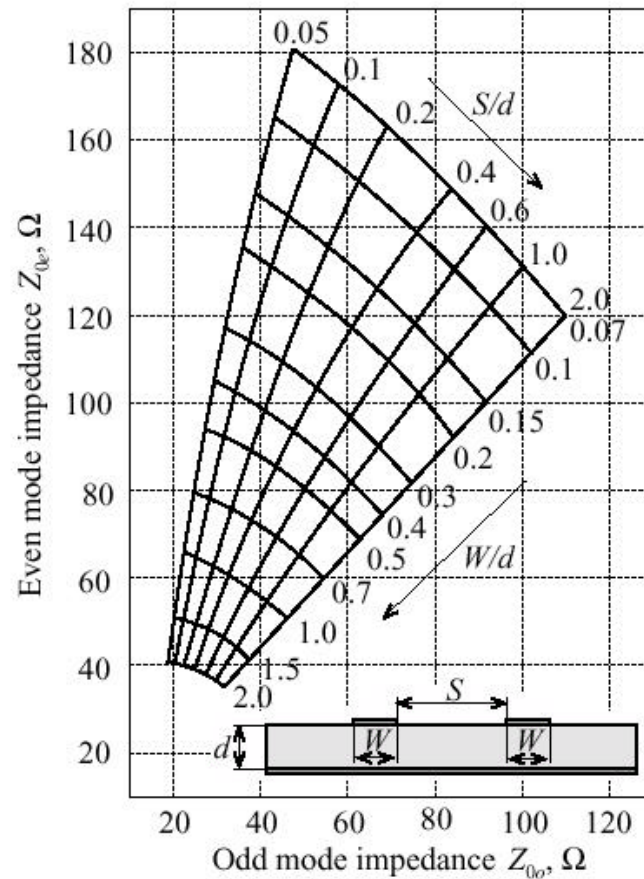

Bandpass Filter Section

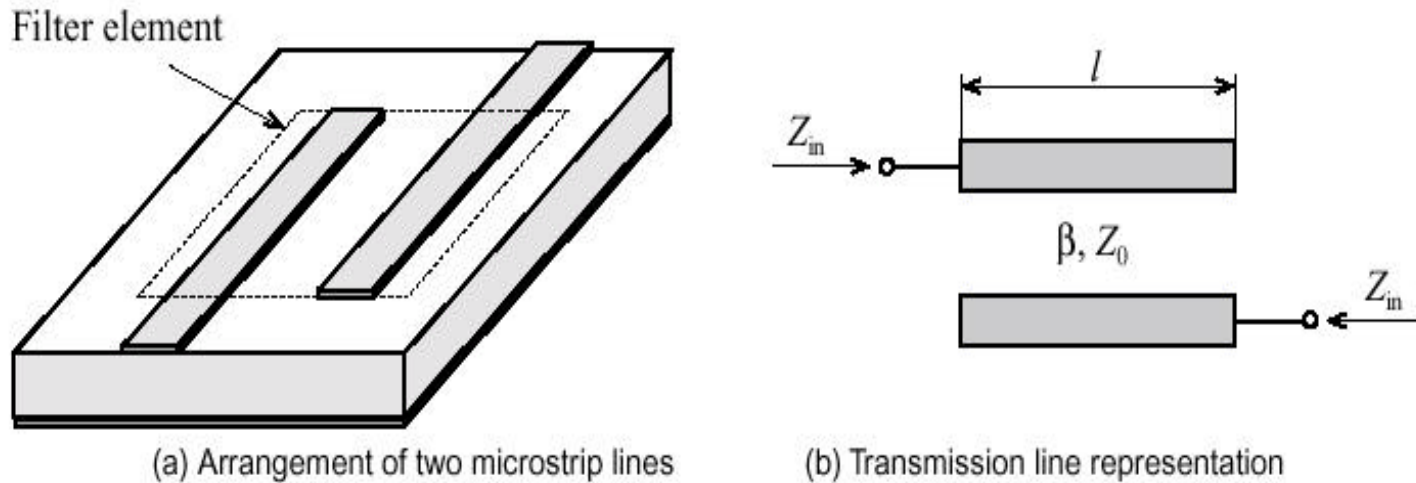


$$Z_{in} = \frac{1}{2 \sin(\mathbf{bl})} \sqrt{(Z_{oe} - Z_{oo})^2 - (Z_{oe} + Z_{oo})^2 \cos^2(\mathbf{bl})}$$

Bandpass Filter Section

- According to Figure 5-47, the characteristic bandpass filter performance attained when

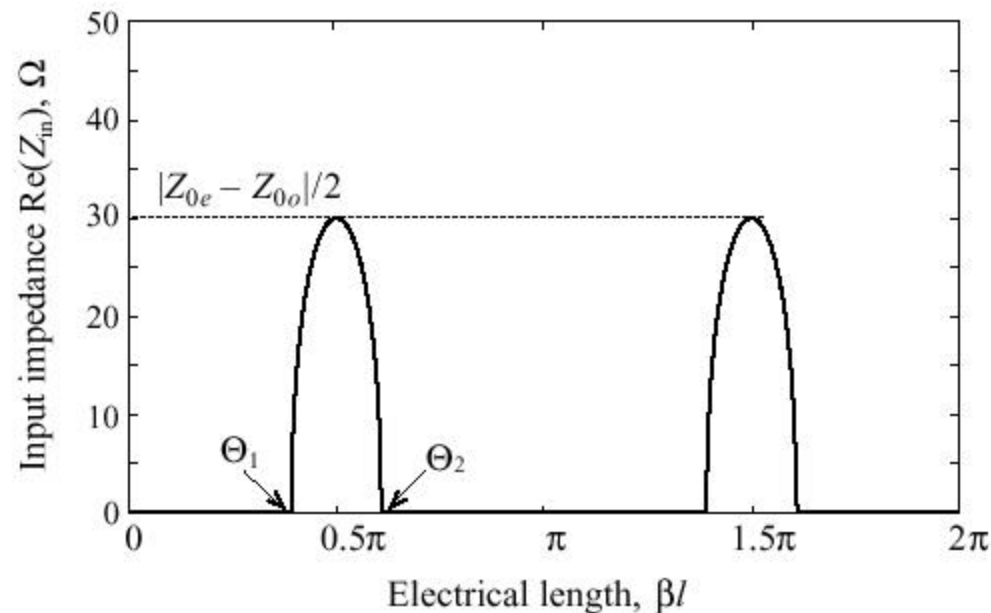
$$l = \mathbf{l} / 4 \text{ or } \mathbf{b} l = \mathbf{p} / 2 .$$



Bandpass Filter Section

- The upper and lower frequencies are
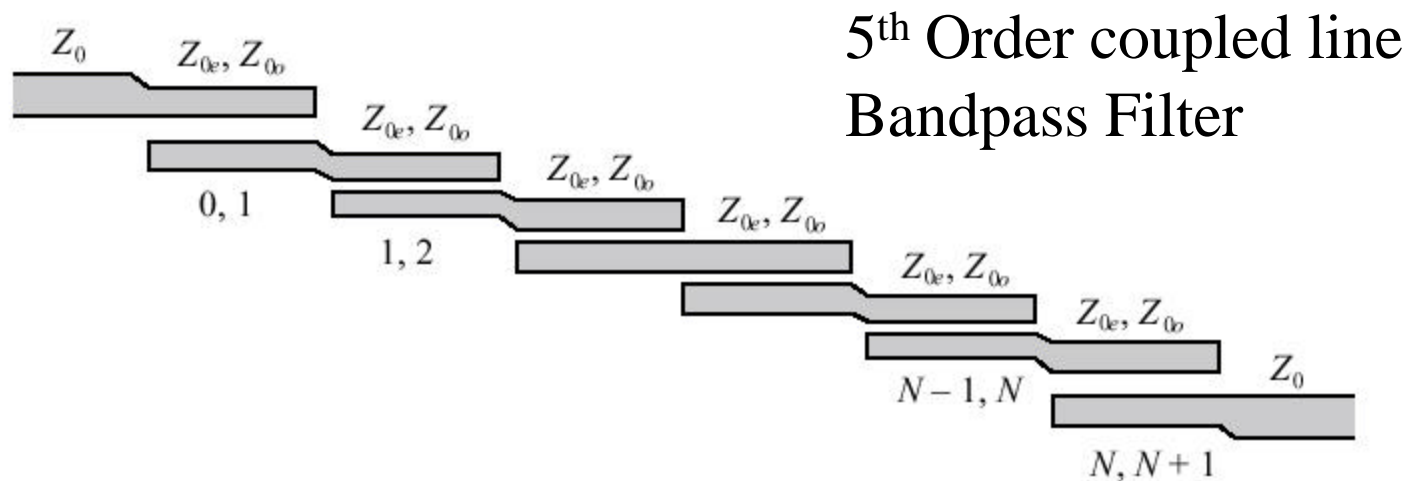
$$(\mathbf{bl})_{1,2} = \mathbf{q}_{1,2} = \pm \cos^{-1} \left[\frac{Z_{0e} - Z_{0o}}{Z_{0e} + Z_{0o}} \right]$$



Bandpass Filter: Implementation

1. Find the low-pass filter prototype
2. Identify normalized bandwidth, upper, and lower frequencies

$$BW = \frac{W_U - W_L}{W_O}$$

- Allowing:

$$J_{0,1} = \frac{1}{Z_O} \sqrt{\frac{pBW}{2g_0g_1}}; \quad J_{i,i+1} = \frac{1}{Z_O} \frac{pBW}{2\sqrt{g_i g_{i+1}}}; \quad J_{N,N+1} = \frac{1}{Z_O} \sqrt{\frac{pBW}{2g_N g_{N+1}}}$$

Bandpass Filter: Implementation

- This allows determination of the odd and even characteristic line impedances:

$$Z_{Oo}|_{i,i+1} = Z_O \left[1 - Z_O J_{i,i+1} + (Z_O J_{i,i+1})^2 \right]$$

and

$$Z_{Oe}|_{i,i+1} = Z_O \left[1 + Z_O J_{i,i+1} + (Z_O J_{i,i+1})^2 \right]$$

- Indices i , $i+1$ refer to the overlapping elements and Z_O is impedance at ends of the filter structure

Bandpass Filter: Implementation

- Determine line dimensions and S and W of the coupled lines from the graph on Figure 5-45 p256.
- Length of each coupled line segment at the center frequency is $l/4$.
- Normalized frequency is

$$\Omega = \frac{w_c}{w_U - w_L} \left(\frac{w}{w_c} - \frac{w_c}{w} \right)$$